

WTF - What the Fuzz

What the Fuzz

December 2015

A handmade fuzz/distortion guitar pedal built from scratch on perfboard and housed in a custom **1590B enclosure** (got some help drilling the holes for that one).

It has **two potentiometers** — one for volume and another for gain — plus **two toggle switches** that change between different diode clipping types, giving a range of fuzz and distortion tones.

The clipping options include **germanium**, **LED**, and **standard silicon** diodes, each with its own character — from smooth, vintage fuzz to aggressive, modern distortion. It also features a **3PDT footswitch** for **true bypass**, and the circuit only powers up when a guitar is plugged in, using the **extra contact on the 6.3 mm jack** to switch power.

Notes:

- Fuzz/distortion effect pedal
- Perfboard build inside custom 1590B enclosure
- Volume and gain controls
- Switchable diode clipping (germanium, LED, silicon)
- 3PDT true bypass
- Auto power via input jack
- 9V powered